

Presentation Topic

Name of the course :- Basic Electronics Engineering

Faculty Name:- Smita Bhagwat- Bannapure

Faculty official (VIIT) mail Id:- smita.bhagwat@viit.ac.in

Department of E&TC Engineering



BRACT'S, Vishwakarma Institute of Information Technology, Pune-48

(An Autonomous Institute affiliated to Savitribai Phule Pune University)
(NBA and NAAC accredited, ISO 9001:2015 certified)

Unit – 03:Field-Effect Transistor (MOSFET) & Power Devices

Mrs. Smita Bhagwat Bannapure

Assistant Professor

Department of E&TC

VIIT, Pune-411048



Acknowledgement

- All figures and text in this presentation are taken from book “**Electronic Devices – Conventional Current Version,**” 9th Ed., by Thomas L. Floyd.

Outline

- Difference between BJT and FET
- E-MOSFET
- Construction,
- Working
- Characteristics
- Biasing techniques and CS Amplifier
- Power Devices- SCR and TRIAC
- Construction,
- Working
- Characteristics
- Application



Difference Between BJT and FET

- BJT: Bipolar and FET: Unipolar
- BJT: Current controlled, FET: Voltage Controlled
- FETs are more temperature stable than BJT
- Size of FET is smaller than BJT
- High Input impedance and offer low gain

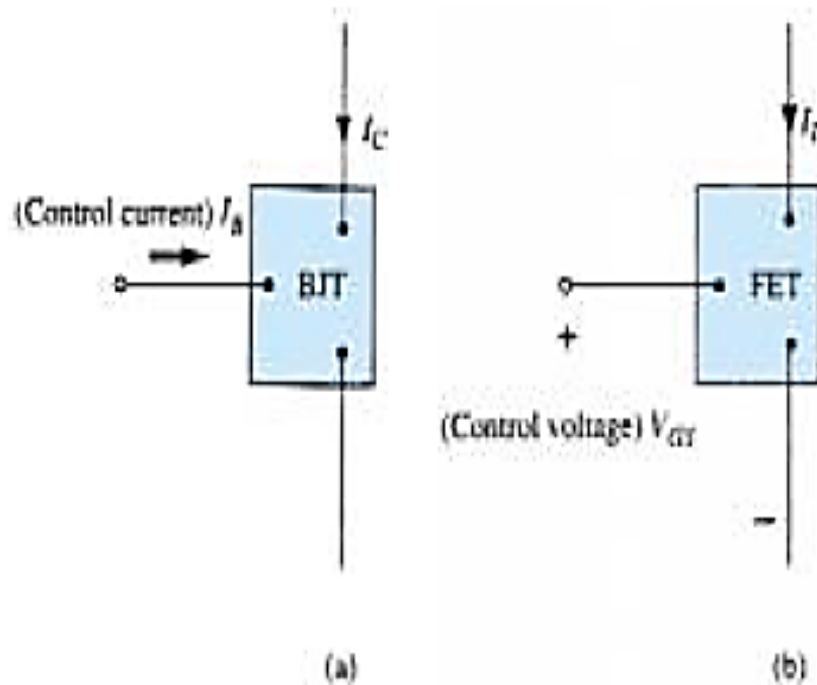


Figure 5.1 (a) Current-controlled and (b) voltage-controlled amplifiers.



Field Effect Transistor (FET): Introduction

- Types of FETs :
 - Junction field-effect transistor (JFET)*
 - metal-oxide-semiconductor field-effect transistor (MOSFET).*
- Types of MOSFET:
 - depletion D-MOSFET
 - enhancement E-MOSFET
- In FET: An *electric field* control the conduction path of the output current
- The MOSFETs are popular in the design and construction of integrated circuits (ICs) for digital computers.
- Its thermal stability and low power dissipation makes it extremely popular in computer circuit design and in VLSI technology



EMOS-FET (Metal Oxide Semiconductor Field Effect Transistor) : Construction

N-channel Enhancement- MOSFET

- A slab of p -type silicon substrate and two n -type regions forming the source and drain terminals are connected through metallic contacts to n -doped regions,
- The channel is absent between the two n -doped regions.
- The SiO_2 layer is present to isolate the gate metallic platform from the region between the drain and source


 


Figure 5.31 n-Channel enhancement-type MOS

 

E-MOSFET: Symbols and Water Analogy



- N-channel EMOSFET
- With V_{DS} at +ve voltage,
- V_{GS} at 0 V,
- SS connected to the source,
- There are two reverse-biased $p-n$ junctions between the n -doped regions and the p -substrate to oppose the I_{DS}
- The absence of an n -channel will result in a zero current.


 


Figure 5.31 n-Channel enhancement-type MOSFET.

Channel Formation in E-MOSFET

- V_{DS} and V_{GS} are positive voltage greater than 0 V, establishing the drain and gate at a positive potential with respect to the source.
- The positive potential at the gate will pressure the holes (since like charges repel) in the p -substrate along the edge of the SiO_2 layer to leave the area and enter deeper regions of the p -substrate.
- However, the electrons in the p -substrate will be attracted to the positive gate and accumulate near the SiO_2 layer.

 

- The insulating property of SiO_2 layer will prevent the electrons from being absorbed at the gate terminal.
- As V_{GS} increases, the concentration of electrons near the SiO_2 surface increases until the induced n -type region can support a measurable flow between drain and source.
- The level of V_{GS} that results in the significant increase in drain current is called the *threshold voltage* (V_T).
- Since the channel is nonexistent with $V_{GS} = 0 \text{ V}$ and “enhanced” by the application of a positive gate-to-source voltage, this type of MOSFET is called an *enhancement-type MOSFET*.



Recap


- Difference between BJT and FET
- Introduction to FET and its types
- Construction of E-MOSFET
- Working of E-MOSFET

Points to be covered

- Pinch-off process
- Transfer characteristics
- Drain Characteristics
- P-channel E-MOSFET
- Configurations (CS, CG, CD)

Fig. Pinch-Off Process
 
$$V_{GS} > V_T \text{ and } V_{DS} > V_{DS(sat)}$$



- The density of free carriers in the induced channel will increase, which increases drain current.
- However, if $V_{GS} = \text{constant}$ and increase the level of $V_{DS} > (V_{GS} - V_{GSTh})$, the drain current will eventually reach a saturation level
- The leveling off of I_D is due to a pinching-off process depicted by the narrower channel at the drain end of the induced channel as shown in Fig.

As $V_{DS} > (V_{GS} - V_T)$, Voltage V_{DG} increases.

- The gate will become less and less positive with respect to the drain.
- This reduction in Gate voltage reduces the attractive forces for free carriers (electrons) in this region of the induced channel, causing a reduction in the effective channel width.
- Eventually, the channel will be reduced to the point of pinch-off and a saturation condition will be established
- In other words, any further increase in V_{DS} at the fixed value of V_{GS} will not affect the saturation level of I_D until breakdown conditions are encountered.

Transfer Characteristics

 



Figure 6.35 Transfer characteristics of an n -channel enhancement-type MOSFET.



$$I_D = k(V_{GS} - V_{GS(Th)})^2$$

Calculation of parameter k

NMOS Transistor (p. 249):

 

Calculation of transconductance parameter k

- W =width of Channel, L =length of Channel
- μ = mobility of charge carriers
- C_{ox} =Capacitance of oxide layer

$$k'_n(W/L) = \mu_n C_{ox}(W/L) = k_n \quad (\text{n-channel}) \text{ and}$$

$$k'_p(W/L) = \mu_p C_{ox}(W/L) = k_p \quad (\text{p-channel}).$$

Drain Characteristics

$$V_{DSsat} = V_{GS} - V_T$$

$$V_{DG} = V_{DS} - V_{GS}$$

 


Figure 5.34 Drain characteristics of an n -channel enhancement-type MOSFET with $V_T = 2$ V and $k = 0.278 \times 10^{-3} \text{ A/V}^2$.

Drain Characteristics

- For a fixed value of V_T , and the higher the level of V_{GS} , the saturation level for V_{DS} is *also more*, as shown by the locus of saturation levels.

$$V_{DS_{sat}} = V_{GS} - V_T$$

- In fact, the saturation level for V_{DS} is related to the level of applied V_{GS} by applying Kirchhoff's voltage law to the terminal voltages of the MOSFET.

$$V_{DG} = V_{DS} - V_{GS}$$

For $V_{GS} < V_T$, $I_D = 0\text{mA}$

The spacing between the levels of V_{GS} increased as the magnitude of V_{GS} increased, resulting in ever-increasing increments in drain current.

$$I_D = k(V_{GS} - V_T)^2$$

- The squared term results in the nonlinear (curved) relationship between I_D and V_{GS} .
- The k term is a constant that is a function of the construction of the device.
- The value of k can be determined from the following equation where $I_D(\text{on})$ and $V_{GS}(\text{on})$ are the values for each at a particular point on the characteristics of the device.

Calculation of k from datasheet values (Example)

$V_T = 2\text{V}$, $I_{D(\text{on})} = 10\text{mA}$, $V_{GS(\text{on})} = 8\text{V}$, $V_{GS} = 4\text{V}$

$$k = \frac{I_{D(\text{on})}}{(V_{GS(\text{on})} - V_T)^2} \quad (5.14)$$

Substituting $I_{D(\text{on})} = 10\text{ mA}$ when $V_{GS(\text{on})} = 8\text{ V}$ from the characteristics of Fig. 5.34 yields

$$\begin{aligned} k &= \frac{10\text{ mA}}{(8\text{ V} - 2\text{ V})^2} = \frac{10\text{ mA}}{(6\text{ V})^2} = \frac{10\text{ mA}}{36\text{ V}^2} \\ &= 0.278 \times 10^{-3}\text{ A/V}^2 \end{aligned}$$

and a general equation for I_D for the characteristics of Fig. 5.34 results in:

$$I_D = 0.278 \times 10^{-3} (V_{GS} - 2\text{ V})^2$$

Substituting $V_{GS} = 4\text{ V}$, we find that

$$\begin{aligned} I_D &= 0.278 \times 10^{-3} (4\text{ V} - 2\text{ V})^2 = 0.278 \times 10^{-3} (2)^2 \\ &= 0.278 \times 10^{-3} (4) = 1.11\text{ mA} \end{aligned}$$

p-Channel Enhancement-Type MOSFETs

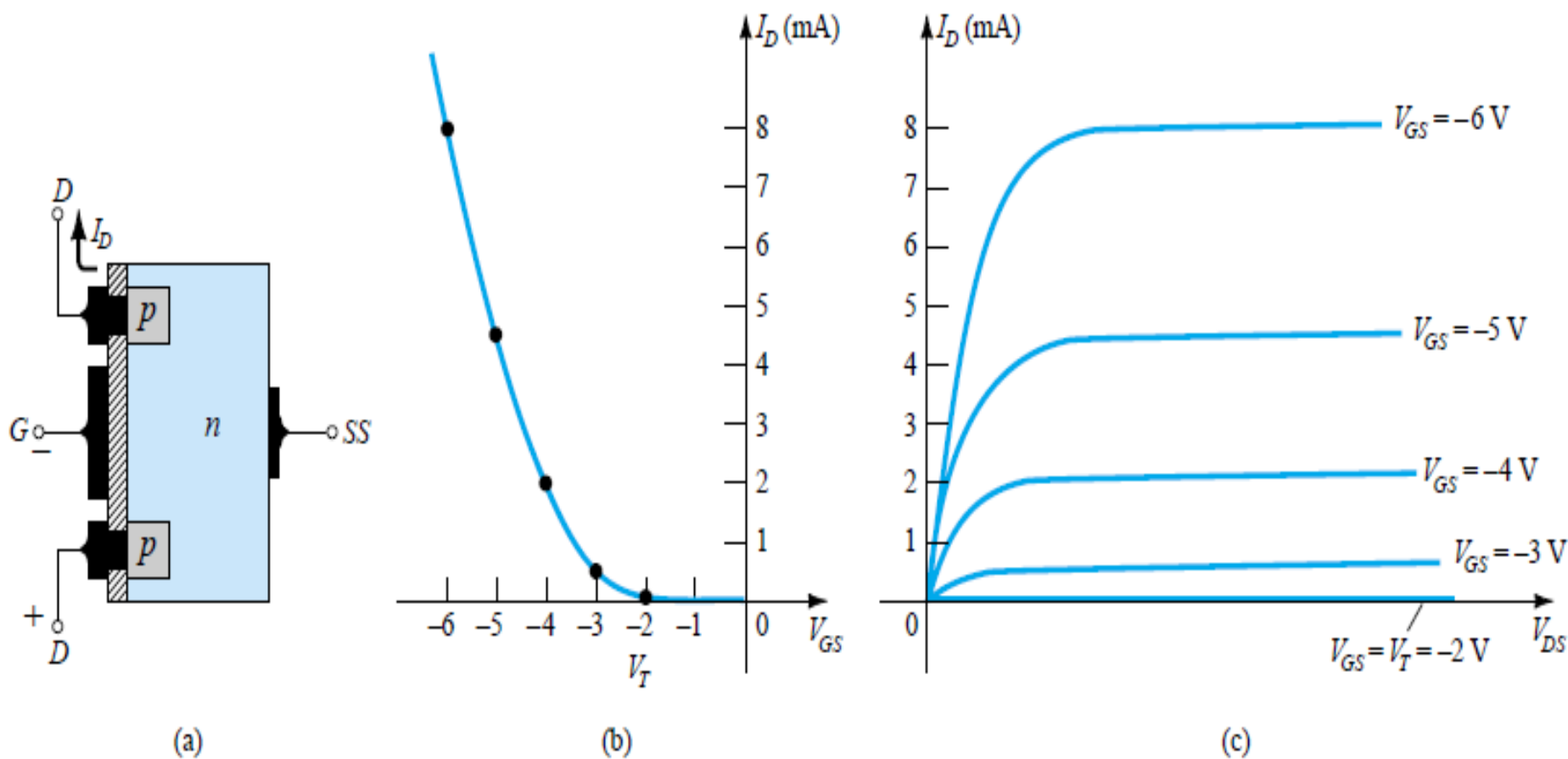


Figure 5.37 p-Channel enhancement-type MOSFET with $V_T = 2$ V and $k = 0.5 \times 10^{-3}$ A/V².

Example 2

The datasheet (see www.fairchild.com) for a 2N7002 E-MOSFET gives $I_{D(on)} = 500 \text{ mA}$ (minimum) at $V_{GS} = 10 \text{ V}$ and $V_{GS(th)} = 1 \text{ V}$. Determine the drain current for $V_{GS} = 5 \text{ V}$.

■ Solution

First, solve for K using Equation 8–4.

$$K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{500 \text{ mA}}{(10 \text{ V} - 1 \text{ V})^2} = \frac{500 \text{ mA}}{81 \text{ V}^2} = 6.17 \text{ mA/V}^2$$


Next, using the value of K , calculate I_D for $V_{GS} = 5 \text{ V}$.

$$I_D = K(V_{GS} - V_{GS(th)})^2 = (6.17 \text{ mA/V}^2)(5 \text{ V} - 1 \text{ V})^2 = 98.7 \text{ mA}$$


The datasheet for an E-MOSFET gives $I_{D(on)} = 100 \text{ mA}$ at $V_{GS} = 8 \text{ V}$ and $V_{GS(th)} = 4 \text{ V}$. Find I_D when $V_{GS} = 6 \text{ V}$.

MOSFET amplifier configurations


Three Basic configurations

 

(a) Common Source (CS)

 

(b) Common Gate (CG)

 

(c) Common Drain (CD)

Source follower

Comparison

Table 11-1 Comparison of common-source, common-drain, and common-gate circuits.

Circuit configuration	Z_i	Z_o	A_v	Phase shift
CS	$\approx R_G$	$\approx R_D$	$-Y_{fs}(R_D \parallel R_L)$	180°
CD	$\approx R_G$	$\approx 1/Y_{fs}$	≈ 1	0
CG	$\approx 1/Y_{fs}$	$\approx R_D$	$Y_{fs}(R_D \parallel R_L)$	0


Summary

- Common-Source (CS) configuration
 - best suited for the *bulk of gain*
- Common-Source (CS) configuration with R_s in the source
 - improved performance but *reduced* gain
- Common-Gate (CG) configuration
 - low input resistance
 - excellent high-frequency performance
 - unity-gain current amplifier
 - *cascode amplifier*
- Common-Drain (CD) or *Source follower*
 - *voltage buffer* for connecting a high-resistance source to
 - a low -resistance load
 - output stage in a multi-stage amplifier

Biasing Technique

Voltage Divider Bias

 - E-MOSFETs must have a $V_{GS} > V_{GS(th)}$,



(a) Voltage-divider bias


$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$V_{DS} = V_{DD} - I_D R_D$$

Example 2:

Determine V_{GS} and V_{DS} for the E-MOSFET circuit in Figure 8–47. Assume this particular MOSFET has minimum values of $I_{D(on)} = 200 \text{ mA}$ at $V_{GS} = 4 \text{ V}$ and $V_{GS(th)} = 2 \text{ V}$.

► FIGURE 8–47

 

For the E-MOSFET in Figure 8–47, the gate-to-source voltage is

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{15 \text{ k}\Omega}{115 \text{ k}\Omega} \right) 24 \text{ V} = 3.13 \text{ V}$$

To determine V_{DS} , first find K using the minimum value of $I_{D(\text{on})}$ and the specified voltage values.

$$K = \frac{I_{D(\text{on})}}{(V_{GS} - V_{GS(\text{th})})^2} = \frac{200 \text{ mA}}{(4 \text{ V} - 2 \text{ V})^2} = \frac{200 \text{ mA}}{4 \text{ V}^2} = 50 \text{ mA/V}^2$$

Now calculate I_D for $V_{GS} = 3.13 \text{ V}$.

$$\begin{aligned} I_D &= K(V_{GS} - V_{GS(\text{th})})^2 = (50 \text{ mA/V}^2)(3.13 \text{ V} - 2 \text{ V})^2 \\ &= (50 \text{ mA/V}^2)(1.13 \text{ V})^2 = 63.8 \text{ mA} \end{aligned}$$

Finally, calculate V_{DS} .

$$V_{DS} = V_{DD} - I_D R_D = 24 \text{ V} - (63.8 \text{ mA})(200 \Omega) = 11.2 \text{ V}$$

Determine V_{GS} and V_{DS} for the circuit in Figure 8–47 given $I_{D(\text{on})} = 100 \text{ mA}$ at $V_{GS} = 4 \text{ V}$ and $V_{GS(\text{th})} = 3 \text{ V}$.

Example 3:

The datasheet (see www.fairchild.com) for a 2N7002 E-MOSFET gives $I_{D(on)} = 500 \text{ mA}$ (minimum) at $V_{GS} = 10 \text{ V}$ and $V_{GS(th)} = 1 \text{ V}$. Determine the drain current for $V_{GS} = 5 \text{ V}$.

First, solve for K using Equation 8–4.


$$K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{500 \text{ mA}}{(10 \text{ V} - 1 \text{ V})^2} = \frac{500 \text{ mA}}{81 \text{ V}^2} = 6.17 \text{ mA/V}^2$$

Next, using the value of K , calculate I_D for $V_{GS} = 5 \text{ V}$.

$$I_D = K(V_{GS} - V_{GS(th)})^2 = (6.17 \text{ mA/V}^2)(5 \text{ V} - 1 \text{ V})^2 = 98.7 \text{ mA}$$

 Example 4:

Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Fig. 6.43.



Figure

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{(18 \text{ M}\Omega)(40 \text{ V})}{22 \text{ M}\Omega + 18 \text{ M}\Omega} = 18 \text{ V}$$

$$V_{GS} = V_G - I_D R_S = 18 \text{ V} - I_D(0.82 \text{ k}\Omega)$$

When $I_D = 0 \text{ mA}$,

$$V_{GS} = 18 \text{ V} - (0 \text{ mA})(0.82 \text{ k}\Omega) = 18 \text{ V}$$

as appearing on Fig. 6.44. When $V_{GS} = 0 \text{ V}$,

$$V_{GS} = 18 \text{ V} - I_D(0.82 \text{ k}\Omega)$$

$$0 = 18 \text{ V} - I_D(0.82 \text{ k}\Omega)$$

$$I_D = \frac{18 \text{ V}}{0.82 \text{ k}\Omega} = 21.95 \text{ mA}$$

 


Figure 6.44 Determining the Q-point for the network of Example 6.12.

$$V_{GS(Th)} = 5 \text{ V}, \quad I_{D(on)} = 3 \text{ mA with } V_{GS(on)} = 10 \text{ V}$$

$$\begin{aligned} \text{Eq. (6.26): } k &= \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2} \\ &= \frac{3 \text{ mA}}{(10 \text{ V} - 5 \text{ V})^2} = 0.12 \times 10^{-3} \text{ A/V}^2 \end{aligned}$$

$$\begin{aligned} I_D &= k(V_{GS} - V_{GS(Th)})^2 \\ &= 0.12 \times 10^{-3} (V_{GS} - 5)^2 \end{aligned}$$


$$I_{DQ} \cong \mathbf{6.7 \text{ mA}}$$

$$V_{GSQ} = \mathbf{12.5 \text{ V}}$$


$$\begin{aligned} \text{Eq. (6.33): } V_{DS} &= V_{DD} - I_D(R_S + R_D) \\ &= 40 \text{ V} - (6.7 \text{ mA})(0.82 \text{ k}\Omega + 3.0 \text{ k}\Omega) \\ &= 40 \text{ V} - 25.6 \text{ V} \\ &= \mathbf{14.4 \text{ V}} \end{aligned}$$

E-MOSFET CS AMPLIFIER

 - A common-source n -channel E-MOSFET with voltage-divider bias with an ac source capacitive coupled to the gate.
- The gate is biased with a positive voltage such that $V_{GS} > V_{GS(th)}$.



 - The signal voltage produces a swing in V_{gs} above and below its Q-point value, V_{GSQ} .
- This, in turn, causes a swing in I_d above and below its Q-point value, I_{DQ} , as illustrated in



he enhancement

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$I_D = K(V_{GS} - V_{GS(th)})^2$$

$$V_{DS} = V_{DD} - I_D R_D$$